

Electronic Circuit Analysis & Design

[Time: Three Hours]

MAY - 18

[Marks: 80]

N.B:

1. Question No. 1 is compulsory.
2. Attempt any Three out of remaining four questions.
3. Assume any suitable data wherever requested but justify the same.

Q.1.

Attempt any 4

a) Draw V-I characteristics of P-N junction diode and explain how Zener diode characteristics differs from that of P-N junction diode.

b) Find IC and VCE for circuit shown below

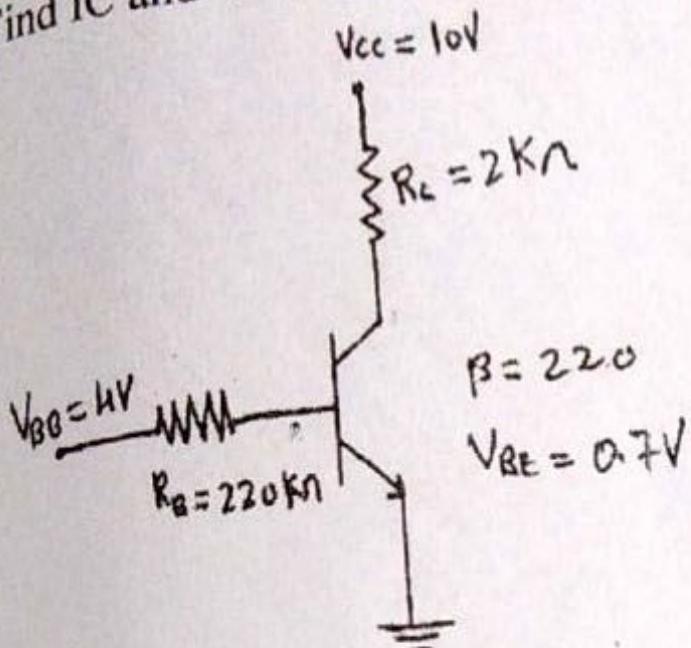


Fig 1

- c) Justify "CB amplifier has larger bandwidth than CE amplifier."
- d) Derive the condition for zero temperature drift in JFET.
- d) Explain the need of cascaded amplifier and list various types of cascaded configurations.

20

20

Q.2. Attempt the following questions :

- a) Derive expression for current stability factor in case of fixed bias and voltage divider bias for BJT.
- b) Find A_v , Z_i , and Z_o for following circuit

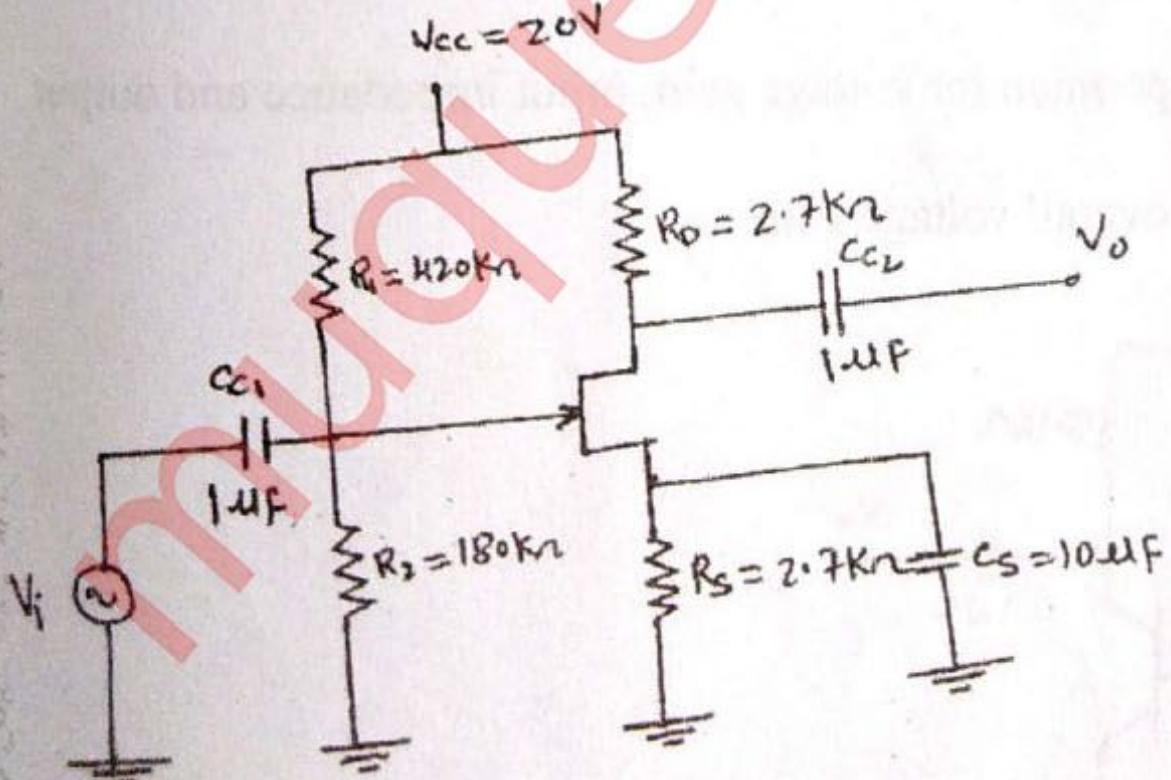


Fig 2

Given : $IDSS = 12mA$, $V_p = 4V$ and $Y_d = 41.7k\Omega$

Q.3. Attempt the following questions :

- a) Draw the structure of MOSFET (E-type, n-Channel) and explain its operation under
 i) Cut-off region
 ii) Linear region
 iii) Saturation region

b) Find ICQ and VCEQ for the circuit given below if $\beta = 100$ and $V_{BE} = 0.7V$

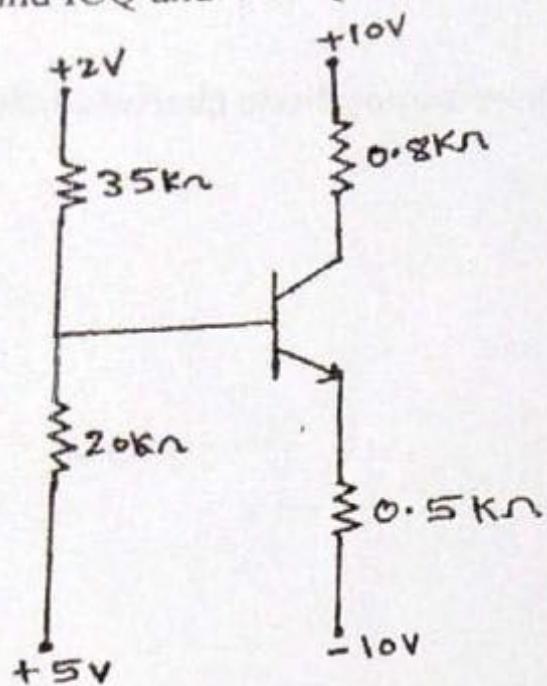


Fig 3

Q.4. Attempt the following questions:

- a) Design a single stage RC coupled CE amplifier to meet the following specification :

$$V_{op} = 3V$$

$$|Av| \geq 120$$

$$S_{ICO} \leq 8$$

$$f_L \text{ better than } 20H_2$$


$$R_i \geq 3K\Omega$$

- b) For amplifier designed in question 4(a), draw small - signal model and calculate Av, ω_i , and ω_o .

Q.5. Attempt the following questions :

- a) Draw cascode amplifier Derive expression for voltage gain, input impedance and output impedance.

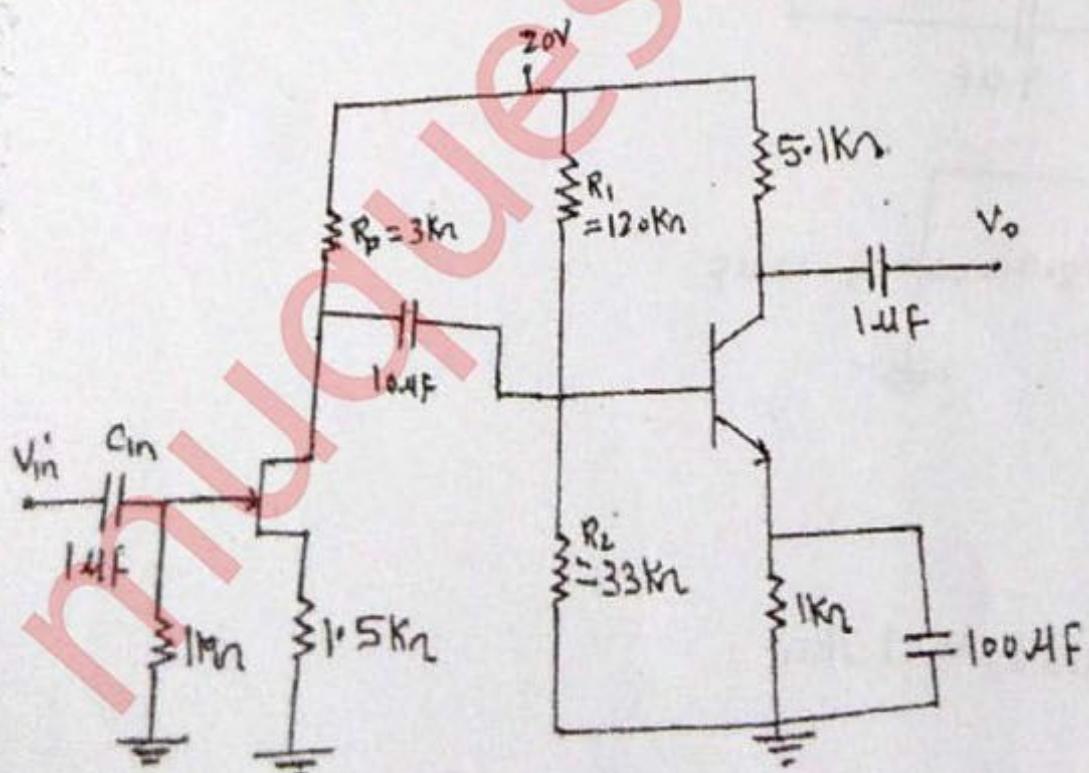- b) For the following circuit calculate overall voltage gain



For JFET : $I_{DSS} = 10mA$, $V_P = -4V$

For BJT : $h_{ie} = 4.5k\Omega$, $h_{fe} = 180$

Write a short note on (any 4) 20

- Q.6.
- a) Self biasing for JFET
 - b) Miller Theorem
 - c) MOSFET applications
 - d) Zener diode
 - e) Darlington Amplifier

S.E / Sem III / BioMed / choice
2/6/18

Board No. 201
Q.P. Code : 40502

DBEC DATA SHEET

Transistor type	P_{dmax} @ 25°C Watts	I_{cmar} @ 25°C Amps	V_{ce} volts d.c.	V_{ceo} volts d.c.	$V_{ce(sus)}$ volts d.c.	V_{ces} volts d.c.	V_{esg} volts d.c.	T_j max °C	D.C. current min	D.C. current typ.	Small signal typ.	k_p	V_{ut} max.	θ_A °CW	Derate above 25°C W/C
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	1.5
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	1.5
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	1.5
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	1.2
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	280	0.9
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	260	0.9
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	45	—	—
											240	330	500	500	0.9
Transistor type			h_{ie}	h_{oe}	h_{re}	h_{je}	h_{joe}								
BC 147A	2.7 KΩ	18 μV	1.5×10^{-4}	$0.4^{\circ}\text{C}/\text{mW}$	—										
2N 525 (PNP)	1.4 KΩ	2.5 μV	3.2×10^{-4}	$0.4^{\circ}\text{C}/\text{mW}$	—										
BC 147B	4.5 KΩ	30 μV	2×10^{-4}	$0.4^{\circ}\text{C}/\text{mW}$	—										
ECN 100	50 Ω	—	—	—	—										
ECN 149	15 Ω	—	—	—	—										
ECN 055	12 Ω	—	—	—	—										
2N 3055	6 Ω	—	—	—	—										

BFW 11-JFET MUTUAL CHARACTERISTICS

$-V_{GS}$ volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
Ios max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
Ios typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
Ios min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V_{ds} max. Volts	V_{dg} max. Volts	P_d max. @25°C	T_j max. °C	I_{DS} (typical)	θ_{J-A}	Derate above 25°C W/C
2N3822	50	50	300 mW	175°C	2 mA	3000 μ A	6 50 KΩ 2 mW
BFW 11 (typical)	30	30	300 mW	200°C	7 mA	5600 μ A	2.5 50 KΩ — 0.59° C/mW