

(3 Hours)

[Total Marks :80]

- N.B. : (1) Question no. 1 is **compulsory**.
 (2) Attempt **any three** questions from remaining **five** questions.
 (3) Assume suitable data if required

1. Solve any five 20
- (a) Convert $(41.62)_8$ to decimal, binary and hexadecimal
 - (b) Compare BJT and FET.
 - (c) Why Zener diode is used as a regulator?
 - (d) Define (i) Slew rate (ii) CMRR. What are the typical values of slew rate and CMRR for Op-amp IC- 741?
 - (e) Convert JK-flip flop to D flip flop
 - (f) What do you mean by Universal gate? Implement Ex-OR gate using NAND gate.
2. (a) What is the need of biasing? Explain Voltage divider bias and locate Q point. 10
 (b) Design half adder using VHDL. 5
 (c) Simplify $AB + B + \overline{AC} + A\overline{B}C$ ($AB + C$)
 $AB + B + \overline{AC} + A\overline{B}C$ ($AB + C$) 5
3. (a) Minimize the following Boolean function using K-map 10
 $F(A, B, C, D) = \sum m(0, 3, 7, 11, 15) + d(1, 2, 5)$
 (b) Explain Differentiator using Op-amp 5
 (c) Explain the working of Liquid Crystal display. 5
4. (a) Design and implement 4 bit binary to gray code converter. 10
 (b) Implement $F(A, B, C, D) = \sum m(1, 2, 5, 11, 14) + d(0, 3)$ using 8:1 multiplexer. 5
 (c) Explain inverting amplifier using Op-amp. Derive expression for output voltage. 5
5. (a) Explain the working of astable multivibrator using IC-555. Design astable multivibrator for output frequency 5KHz and duty cycle 30%. 10
 (b) Differentiate between combinational and sequential logic circuits. 5
 (c) Design mod-3 up counter using JK flip-flop 5
6. Write notes on Any four :- 20
- (a) Instrumentation amplifier using 3-OP-Amps.
 - (b) Shift registers.
 - (c) Race around condition.
 - (d) Current mirror circuit.
 - (e) Multiplexers and De multiplexers.