

[Time: 3 Hours]

[Total Marks: 80]

Instructions:

1. Question No: 1 is compulsory.
2. Answer any three from the remaining five questions.

- 1 (5 x 4)
- a) Explain the working of full wave bridge rectifier circuit with neat waveforms.
 - b) Interpret the V-I characteristics of MOSFET.
 - c) Draw and explain the frequency response of BJT amplifiers.
 - d) Illustrate the working of Schottky diode with its applications.
- 2 (10)
- a) Illustrate with a neat figure, derive the expression of output voltage of subtractor circuit using op-amp.
 - b) Draw the hybrid equivalent model of voltage divider bias CE amplifier and derive the expression for voltage gain. (10)
- 3 (10)
- a) Illustrate any three biasing circuits employed in MOSFET amplifiers. (10)
 - b) Explain the working of Astable multivibrator using IC555. (10)
- 4 (10)
- a) Illustrate the procedure to find I_{CQ} and V_{CEQ} for an emitter bias BJT Amplifier with an example. (10)
 - b) Illustrate the working MOSFET CS amplifier. Derive the expression of voltage gain. (10)
- 5 (10)
- a) Explain the construction and working of optoisolators. (10)
 - b) Explain the working of op-amp as instrumentation amplifier. (10)
- 6 (20)
- Write short notes:
- 1) LED and Zener diodes.
 - 2) Inverting and Non-inverting amplifier using op-amp.
