

Time: 3 Hrs

Marks: 80


Note:

- Question No. 1 is compulsory.
- Answer any **three** from the remaining five questions.
- Assume suitable data if necessary and justify the same.

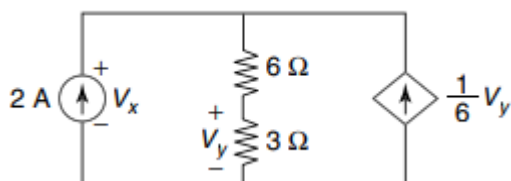
Q1 Each question carries five marks

20M

- a The voltage $V(s)$ of a network is given by $V(s) = \frac{(s+8)(s+10)}{(s+4)(s^2+2s+2)}$ Plot its pole-zero diagram
- b Find the voltage ' V_x ' in the following circuit



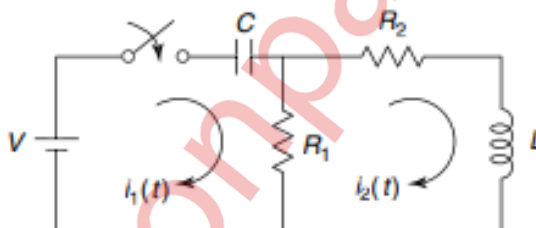- c The Z-parameters of a two-port network are: $Z_{11} = 12 \Omega$, $Z_{12} = Z_{21} = 8 \Omega$, $Z_{22} = 20 \Omega$. Find the equivalent T-network.
- d In the network shown, the switch is closed at $t = 0$, assuming all initial conditions as zero, determine the current $i_1(0^+)$ and $i_2(0^+)$.



Q2 a The reduced incidence matrix of an oriented graph is


10M

$$A = \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 1 & 0 \end{bmatrix}$$


(a) Draw the graph. (b) How many trees are possible for this graph? (c) Write the tieset and cutset matrices.

b Find the voltage V and verify reciprocity theorem for the network shown.


10M

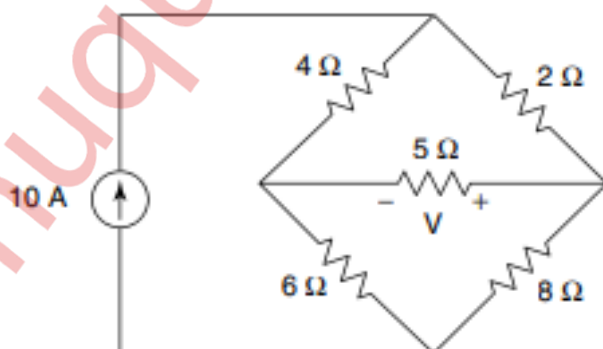

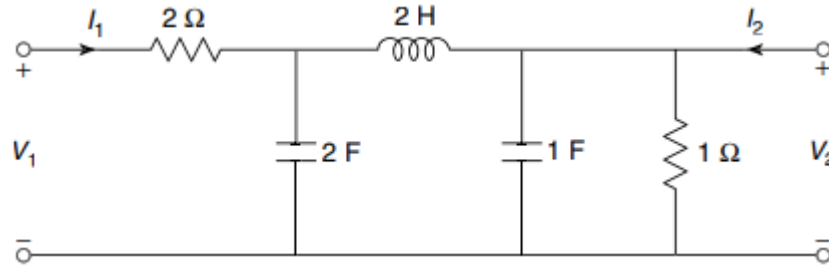
Q3 a Obtain h-parameters of the network shown 10M



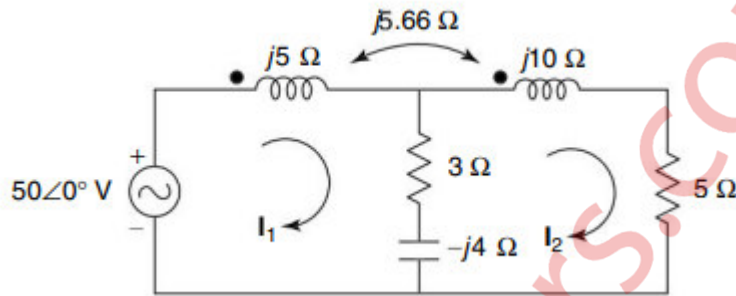b Determine the voltage across the 3Ω resistor using mesh analysis. 10M




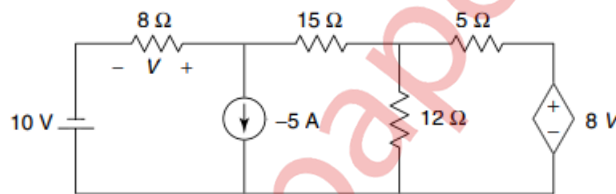Q4 a Find the voltage V using Thevenin's theorem. 10M




b Derive the condition for reciprocity and symmetry for Y-parameters. 10M

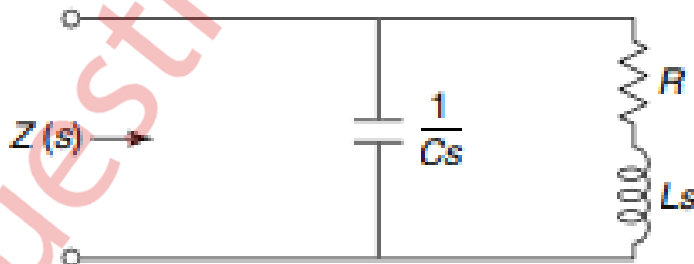
Q5 a For the given network, poles and zeros of driving point function $Z(s)$ are, poles: $(-1 \pm j2)$; zero: -4 . If $Z(j0) = 1$, find the values of R, L and C. 10M



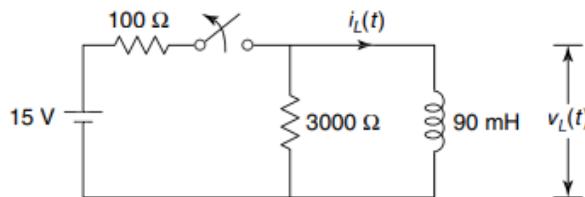b For the following network, steady state is reached with the switch closed. The switch is opened at $t = 0$. Obtain expressions for $i_L(t)$ and $v_L(t)$. 10M



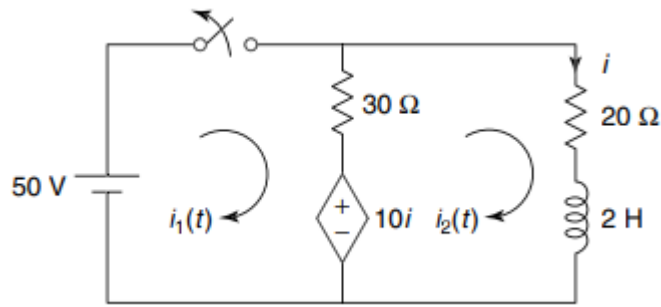- Q6 a For the network shown, find the current in the $20\ \Omega$ resistor when the switch is opened at $t=0$. 10M



- b Determine the transmission parameters of the following network. 10M

